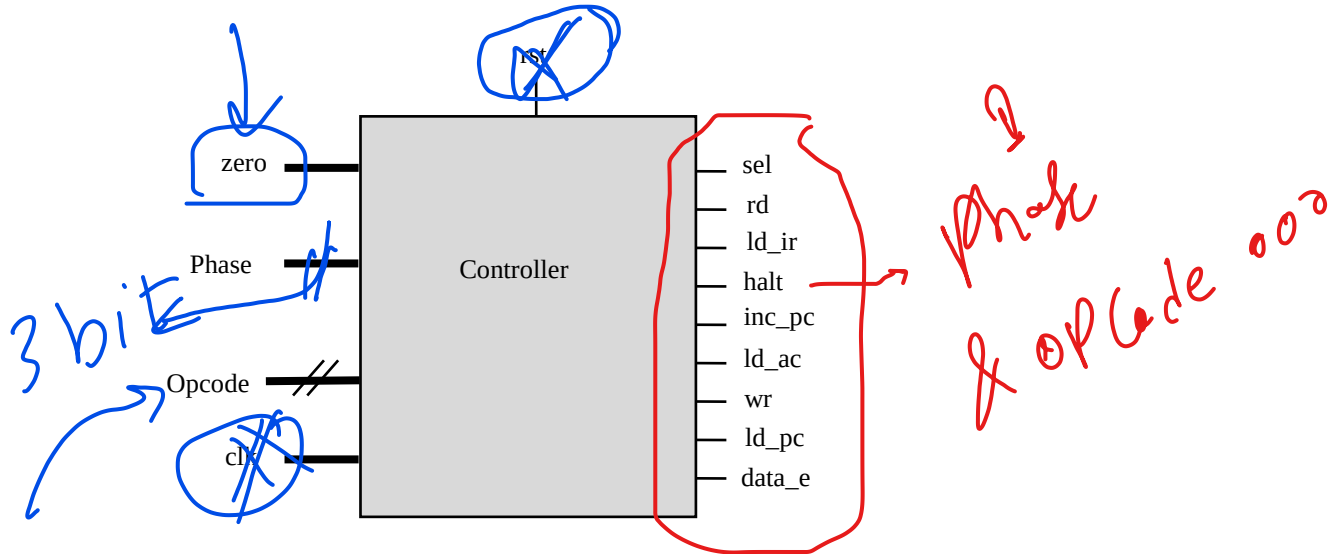


Module 6: Making Procedural Statements

Lab 6-1 Modeling a Controller


Objective: To use the Verilog case statement to describe a controller.

The controller generates all control signals for the VeriRISC CPU. The operation code, fetch-and-execute phase, and whether the accumulator is zero determine the control signal levels.



Specifications

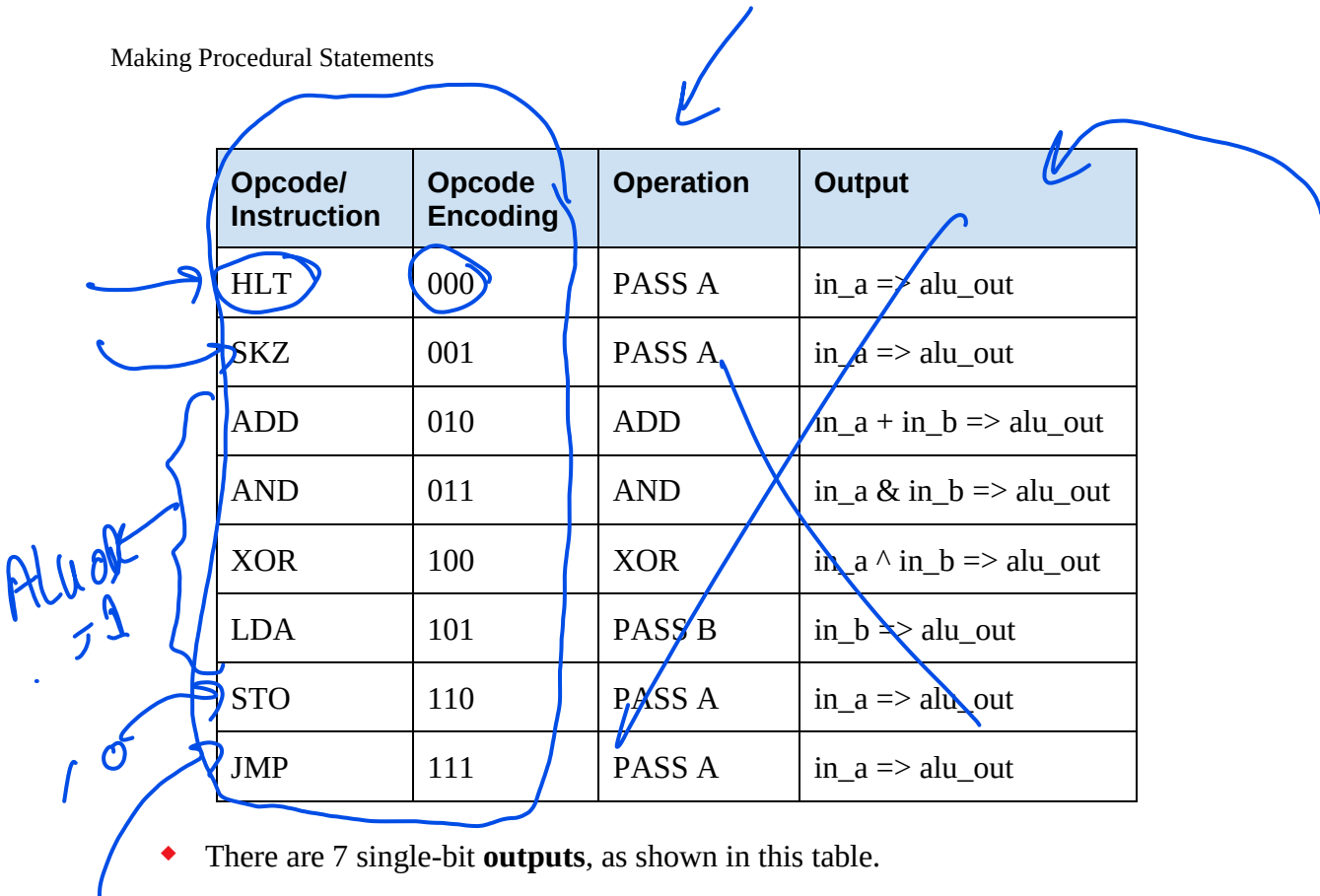- ♦ The controller is clocked on the rising edge of `clk`.
- ♦ `rst` is synchronous and active high.
- ♦ `zero` is an **input** which is 1 when the CPU accumulator is zero and 0 otherwise.
- ♦ `opcode` is a 3-bit **input** for CPU operation, as shown in the following table.



Opcodc/ Instruction	Opcodc Encoding	Operation	Output
HLT	000	PASS A	in_a => alu_out
SKZ	001	PASS A	in_a => alu_out
ADD	010	ADD	in_a + in_b => alu_out
AND	011	AND	in_a & in_b => alu_out
XOR	100	XOR	in_a ^ in_b => alu_out
LDA	101	PASS B	in_b => alu_out
STO	110	PASS A	in_a => alu_out
JMP	111	PASS A	in_a => alu_out


- ♦ There are 7 single-bit **outputs**, as shown in this table.

Output	Function
sel	select
rd	memory read
ld_ir	load instruction register
halt	halt
inc_pc	increment program counter
ld_ac	load accumulator
ld_pc	load program counter
wr	memory write
data_e	data enable

Phase → 9 100.

- The controller has a single-bit phase input with a total of 8 phases processed. Phase transitions are unconditional, i.e., the controller passes through the same 8-phase sequence, from INST_ADDR to STORE, every 8 clk cycles. The reset state is INST_ADDR.

phase 3 bit

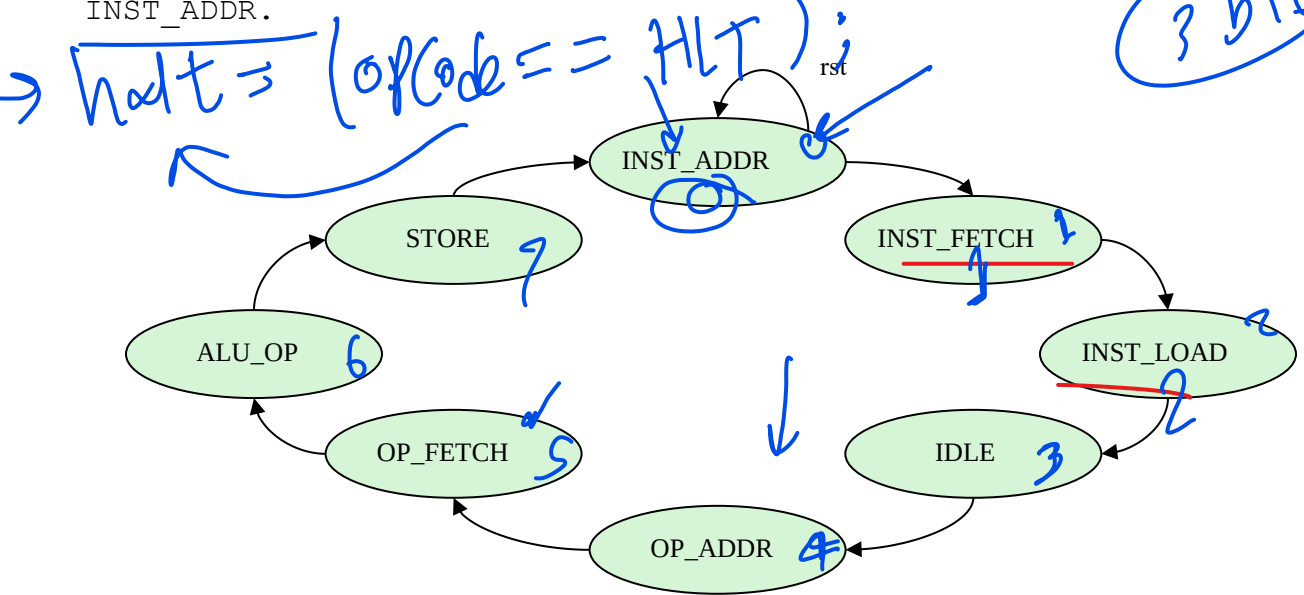

- The controller outputs will be decoded w.r.t phase and opcode, as shown in this table.

Outputs	Phase							Notes	
	INST_ADDR	INST_FETCH	INST_LOAD	IDLE	OP_ADDR	OP_FETCH	ALU_OP	STORE	
sel	1	1	1	1	0	0	0	0	ALU_OP = 1 if opcode is ADD, AND, XOR or LDA
rd	0	1	1	1	0	ALUOP	ALUOP	ALUOP	
ld ir	0	0	1	1	0	0	0	0	
halt	0	0	0	0	HALT	0	0	0	
inc_pc	0	0	0	0	1	0	SKZ & zero	0	
ld ac	0	0	0	0	0	0	0	ALUOP	
ld pc	0	0	0	0	0	0	JMP	JMP	
wr	0	0	0	0	0	0	0	STO	
data_e	0	0	0	0	0	0	STO	STO	

if (Phase == 3'b100)
begin
halt = 1 (opcode == 3'b000);

HALT = (opcode == 3'b000);

Designing a Controller

1. Change to the *lab7-ctrl* directory and examine the following files.

controller_test.v	Controller test
filelist.txt	File listing all modules to simulate

2. Use your favorite editor to create the *controller.v* file and describe the controller module named “*control*”.
3. Declare a reg for each of these intermediate terms and establish their value immediately before entering the case statement.

Verifying the Controller Design

1. Using the provided test module, check your controller design using the following command with Xcelium™.

```
xrun controller.v controller_test.v (Batch Mode)
```

or

```
xrun controller.v controller_test.v -gui -access +rwc ( GUI Mode)
```

2. You might find it easier to list all the files and simulation options in a text file and pass the file into the simulator using the `-f xrun` option.

```
xrun -f filelist.txt -access rwc
```

You should see the following results.

```
Testing opcode HLT phase 0 1 2 3 4 5 6 7
Testing opcode SKZ phase 0 1 2 3 4 5 6 7
Testing opcode ADD phase 0 1 2 3 4 5 6 7
Testing opcode AND phase 0 1 2 3 4 5 6 7
Testing opcode XOR phase 0 1 2 3 4 5 6 7
Testing opcode LDA phase 0 1 2 3 4 5 6 7
Testing opcode STO phase 0 1 2 3 4 5 6 7
Testing opcode JMP phase 0 1 2 3 4 5 6 7
TEST PASSED
```

3. Correct your controller design as needed.

